

Name _____

Date _____

1. Students are experimenting to find out if different types of batteries will affect the brightness of a light bulb. The materials for the investigation are shown below. (5.2.A)




What is the variable in the investigation? *what is being changed?*


- A. the light bulb *1*
- B. the wires *all the same*
- C. the different types of batteries
- D. the metal on the light bulb *not changing*


2. The flow of electricity in circuits requires a complete path through which an electric current can pass. Which of the following can an electric current produce? *What can electricity make?*


- F. light *✓ light bulb*
- G. heat *✓ toaster*
- H. sound *✓ speakers*
- J. all of the above

3. Which of the following does NOT need an electrical circuit to operate correctly?


A.  *Batteries*

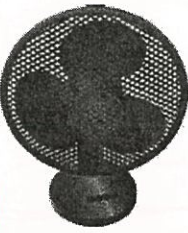B.  *plug*

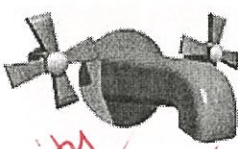C.  *Not electricity X*

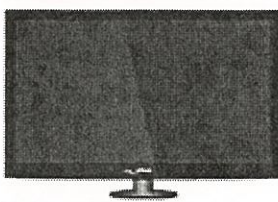D.  *plug*

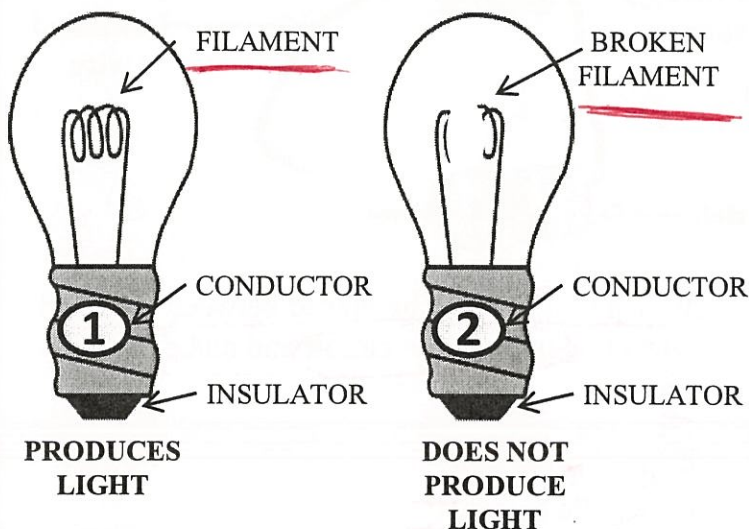
4. The parts of a light bulb work together as a system to produce light. The picture below shows a light bulb that produces light and a light bulb that does not produce light. (5.2.D)



Why does light bulb number two NOT produce light?

- F. The filament is broken and the circuit is open. *✓ does not work*
- G. The filament is not a conductor of electricity. *same*
- H. The filament is an insulator. *same*
- J. The filament is broken and the circuit is closed. *works*

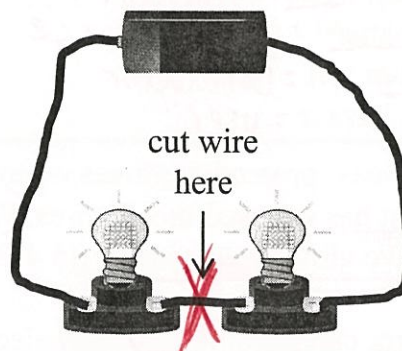5. The picture below shows a complete circuit. *works*




What would happen if the wire was cut between the two light bulbs?

- A. Both bulbs would remain lit. *X open circuit*
- B. Both bulbs would not remain lit. *✓*
- C. Only one bulb would remain lit. *open circuit*
- D. The battery would light up. *?*

Name _____

Date _____

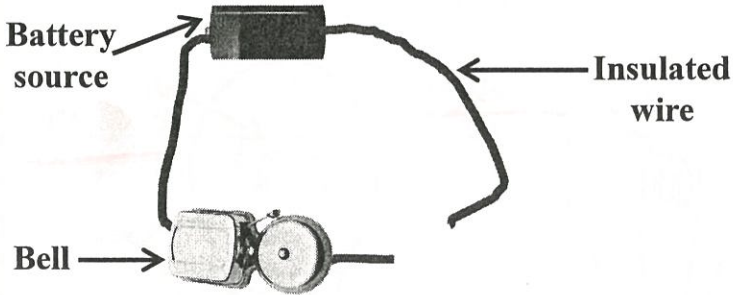6. Students are building complete circuits to test conductors and insulators of electricity. Below is a picture of an open circuit.



Which object could be placed between the open wires to complete the circuit and make the bell ring?

- F. cotton swab *I*
- G. plastic button *I*
- H. glass marble *I*
- J. copper penny *C*


7. Students are given a small electric buzzer, a strip of aluminum foil, a D cell battery, and two insulated wires. If the students build a working circuit that makes the buzzer go off, what is the source of energy for the buzzer?

- A. insulated wires = conductors
- B. D cell battery = power source
- C. aluminum foil = conductor
- D. electric buzzer = user

8. A teacher wears protective gloves when creating a circuit that has exposed metal wires. Why are the protective gloves necessary? ((5.4.B)

- F. The wires can become hot when electricity flows through.
- G. The wires can become cold when electricity flows through.
- H. The gloves help keep the teacher's hands warm.
- J. None of the above.

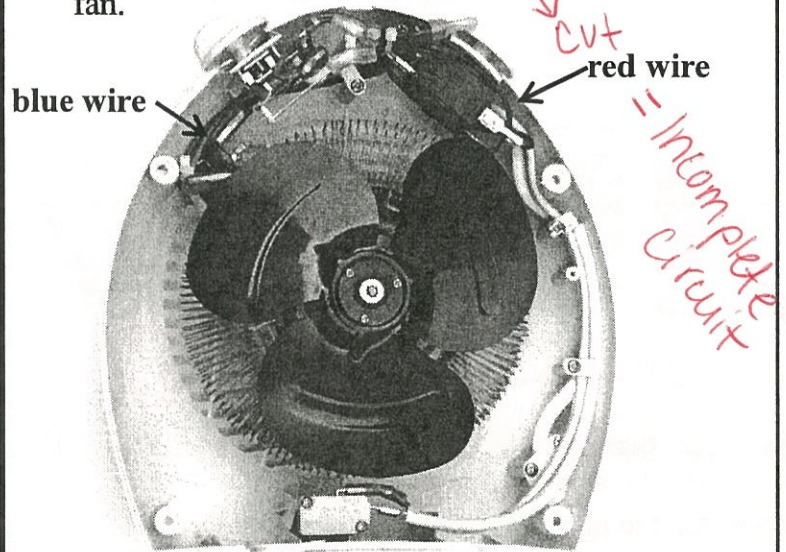
9. Pictured below is a complete circuit in a working fan.



What would happen to the fan if the red wire were cut? (5.2.D)

- A. The fan would spin faster.
- B. The fan would spin slower.
- C. The fan would stop working. *Incomplete circuit*
- D. The fan would produce light. *mechanical energy*

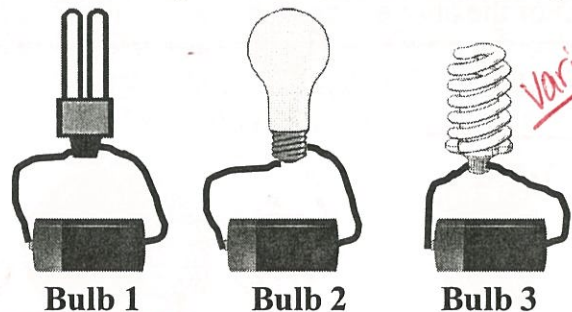10. A student uses three different types of bulbs and builds a complete circuit for each one. (5.2.B)



Which question is this investigation most likely designed to answer?

- F. How do different bulbs react to a simple circuit? *variable*
- G. How do different batteries affect the brightness of a bulb?
- H. How do insulated wires affect a circuit? *wires not mentioned*
- J. How do batteries work in a circuit? *No variable*